

# Index

## A

ABC sequence, 480, 509, 516  
AC; *see* Alternating current  
AC bridges, 381, 382, 391; *see also* Bridge circuit  
AC circuits, 354  
AC sweep, 886  
ACB sequence, 480  
Active filters, 613  
    advantages of, 614  
Admittance, 370, 384, 672  
    definition of, 371  
Aidela, J. B., 929  
Alley, R. E., 930  
Alternating current (ac), 354, 477, 514, 568  
    definition of, 7  
Ammeter, 57, 58  
Ampere, Andre-Marie, 3  
Amplifier  
    averaging type, 194  
    bridge type, 200  
    current type, 200  
    difference type, 177, 190  
    inverting type, 171, 172, 189, 220, 416  
    noninverting type, 174, 189, 419  
    summing type, 176, 189  
    transresistance type, 173  
Amplitude, 355, 384, 880  
Amplitude modulation (AM), 769, 785, 790  
    definition of, 786  
Amplitude spectrum, 711, 735, 762; *see also*  
    Frequency spectrum  
Analog computer, 222  
Angerbaur, G. J., 929  
Angular frequency, 355, 384  
Apparent power, 447, 451, 465, 495, 510, 556  
    definition of, 447  
Argument, 355, 356, 384  
Attributes, 869  
Autotransformer, 552, 570  
    definition of, 553  
Average power, 435, 445, 464, 495, 509, 730, 750; *see also*  
    Real power  
Average value, 444, 708, 710

## B

Balabanian, N., 929  
Balanced load, definition of, 481  
Balanced  $\Delta$ - $\Delta$  system, 488, 557  
Balanced  $\Delta$ -Y system, 490, 557  
Balanced Y- $\Delta$  system, 486, 557

Balanced Y-Y system, 482, 556  
Bandpass filter, 609–611, 615  
    definition of, 611  
Bandstop filter, 609, 611, 616  
    definition of, 611  
Bandwidth, 602, 616, 620, 632  
Bandwidth of rejection, 611  
Barkhausen criteria, 418  
Barkowiak, R. A., 929  
Bell, Alexander G., 588, 707  
Bell, D. A., 929  
Beloved, C., 929  
Blackwell, W. A., 929  
Bobrow, L. S., 929  
Boctor, S. A., 929  
Bode, Henrick W., 589  
Bode plots, 589, 632  
    definition of, 589  
Boylestad, R. L., 929  
Branch, 60  
    definition of, 33  
Break frequency; *see* Corner frequency  
Bridge circuit, 50, 381, 430  
    types of, 391  
Budak, A., 929

## C

Capacitance, 202  
    definition of, 202  
    for parallel combination, 209  
    for series combination, 209  
Capacitance multiplier, 416, 420  
Capacitor, 202, 205, 225  
    applications of, 202–204, 220  
    definition of, 202  
    in parallel, 229  
    properties of, 205, 219  
    in series, 229  
    types of, 203, 205  
    values of, 203  
Carlson, B. A., 929  
Cascade connection, 181, 819  
Cathode-ray tube, 15, 16  
Center frequency, 616  
Characteristic equation, 302  
Charge  
    conservation of, 6  
    definition, 6  
Chattergy, R., 929  
Chen, W. K., 929  
Choudhury, D. R., 929

Cilenti, M. D., 929  
 Circuit, 4, 21  
   analysis of, 4  
   definition of, 4  
 Coefficient of coupling; *see* Coupling coefficient  
 Communication skill, 119  
 Communication system, 759  
 Complete response, 259, 260, 283, 303, 315, 320, 668, 695  
 Completing the square, 661  
 Complex conjugate, 361, 854  
 Complex numbers, 359–361, 851–858  
   in exponential form, 852  
   in polar form, 851  
   in rectangular form, 851  
 Complex power, 449, 451, 465, 495, 517, 548, 553  
 Computer; *see* Analog computer  
 Computer engineering, 237  
 Conductance, 31, 60, 371  
   definition of, 31  
 Conductance matrix, 95  
 Conservation of charge, 6, 35  
 Conservation of energy, 11, 37  
 Conservation of power, 11, 453, 454  
 Control systems, 583  
 Convolution, 677, 695, 771  
   definition of, 677  
   properties of, 678  
 Convolution integral, 677, 695  
   steps for evaluating, 679  
 Corner frequency, 591  
 Coupling; *see* Magnetic coupling  
 Coupling coefficient, 537, 569  
   definition of, 537  
 Cramer's rule, 76, 845  
   definition of, 847  
 Critically damped response; *see* Response  
 Crossover network, 630, 633  
 Cunningham, D. R., 929  
 Current  
   alternating, 7, 21  
   definition, 7  
   direct, 7  
 Current divider, 29, 33, 44, 45  
 Current division, 44, 61, 374  
 Current gain, 585, 672  
 Cutoff frequency, 609

## D

Damping, 305  
 Damping factor, 305, 340, 880  
 Damping ratio, 303  
 d'Arsonval meter movement, 57  
 Davis, A., 929  
 DeCarlo, R. A., 929  
 Decibel (dB), 588  
 Delay circuit, 276  
 Delta function; *see* Unit impulse

Delta-connected load, 492, 486, 489  
 Delta-connected source, 492, 489, 490  
 Delta-wye transformation, 50, 61, 375  
 Del Toro, V., 929  
 Demodulation, 787  
 Derivatives, 861  
 Determinant, 846  
 Direct current, 7, 477, 568  
   definition of, 7  
 DC; *see* Current, direct  
 DC meters, 56  
 DC sweep, 873  
 Difference amplifier; *see* Amplifier  
 Differentiator, 221, 426  
 Digital-to-analog converter, 185  
 Dirichlet, P. G. L., 709  
 Dirichlet conditions, 709  
 Discrete Fourier transform (DFT), 741  
 Dorf, R. C., 929  
 Dot convention, 530, 531, 569  
 Dual circuits, 333, 340  
 Duality, 332, 606, 668, 771  
 Duality principle, 333  
 Durney, C. H., 929

## E

Edison, Thomas A., 477, 478  
 Edminster, J., 929  
 Education, 795  
 Effective value, 443, 464  
   definition of, 443, 444  
 Electric circuit; *see* Circuit  
 Electric current; *see* Current  
 Electric shock, 516  
 Electrical isolation, 553, 564  
 Electricity bill, 17, 22, 462  
 Electromagnetics, 527  
 Electromotive force, 6, 9  
 Electronic instrument, 165  
 Electronics, 75  
 Element, 4  
   active, 13  
   passive, 13  
 Energy, 10, 11  
   conservation of, 11  
   consumption of, 17  
   for coupled coils, 535  
 Equivalence, 127, 132  
 Equivalent circuit, 42, 62, 128, 131, 147, 208, 218, 250, 541, 549  
   of current sources, 37  
   of op amp, 167  
   of voltage sources, 38  
 Euler's formula, 856  
 Even function, 720  
 Excitation, 120, 677

## F

Faraday, Michael, 201, 202  
 Fast Fourier transform (FFT), 741  
 Filters, 584, 632, 746, 751  
   active types, 613  
   applications of, 626, 628, 630  
   bandpass, 609, 610  
   bandstop, 609, 611  
   definition of, 608  
   highpass, 609, 610  
   lowpass, 609  
   passive types, 608, 613  
 Final value, 296, 297, 654  
 Final-value theorem, 655  
 First-order circuit, 238, 282  
   definition of, 238  
   for op amp, 268  
 Flash unit, 278  
 Floyd, T. L., 929  
 Forced response, 259, 314, 315, 320  
   definition of, 260  
 Fourier, J. B. Joseph, 707, 708  
 Fourier analysis, 709  
   with *PSpice*, 740  
 Fourier coefficients, 708, 750  
 Fourier series, 708, 749  
   amplitude-phase form, 711, 730, 750  
   for circuit applications, 727  
   cosine type, 717  
   definition of, 709  
   exponential form, 734, 735, 750, 761  
   sine type, 719  
   trigonometric form, 708, 750  
 Fourier theorem, 708  
 Fourier transform, 760, 762, 789  
   applications of, 785  
   circuit applications of, 779  
   conditions for existence, 763  
   definition of, 762  
   properties of, 766  
 Franco, S., 929  
 Franklin, Benjamin, 6  
 Frequency  
   damping, 305  
   fundamental, 708  
   natural, 303  
   neper, 303  
   resonant, 303  
   undamped natural, 303, 305, 340  
   unit of, 353  
 Frequency differentiation, 653  
 Frequency domain, 363  
 Frequency of rejection, 611  
 Frequency response, 584, 631  
   using *PSpice*, 622, 632, 886  
 Frequency shifting, 651, 769  
 Frequency spectrum, 584, 711, 750  
   definition of, 711  
 Fundamental frequency, 708

## G

Gain  
   closed-loop, 168  
   open-loop, 167  
 Gate function, 253  
 Gibbs, Joseph W., 713  
 Gibbs phenomenon, 713  
 Goody, R. W., 929  
 Grigsby, L. L., 929  
 Grob, B., 929  
 Ground, 76, 77, 515, 516; *see also* Reference node

## H

Half-power frequencies, 602, 632  
 Harmonics, 708  
 Harrison, C. A., 929  
 Harter, J. J., 929  
 Hassul, M., 930  
 Hayt, W. H., 929  
 Hazen, M. E., 929  
 Heaviside, Oliver, 660  
 Heaviside's theorem, 660  
 Henry, Joseph, 201  
 Hermite, M. E., 929  
 Hertz, H. Rudolf, 353, 356  
 Highpass filter, 609, 610, 614, 629, 630  
   definition of, 610  
 Hostetter, G. H., 929  
 Hubert, C. I., 929  
 Huelsman, L. P., 929  
 Hyperbolic functions, 860

## I

IEEE, 295, 353  
 Ignition circuit, 281, 336, 340  
 Impedance, 370, 384, 672  
   definition of, 370  
 Impedance matching, 548, 566  
 Impulse response, 673, 695, 780  
 Induced voltage; *see* Mutual voltage  
 Inductance, 528  
   definition of, 212  
   parallel combination, 333, 217  
   series combination, 333, 216  
 Inductance simulator, 430  
 Inductor, 202, 211, 226  
   applications of, 211, 219  
   definition of, 212  
   properties of, 213, 214, 219  
   values of, 212  
 Initial conditions, 667  
 Initial value, 296, 297, 654

Initial-value theorem, 655  
 Instantaneous power, 10, 434, 494, 517  
 Instrumentation amplifier, 177, 187  
 Integrals, 861–863  
 Integration by parts, 861  
 Integrator, 220, 428  
 Integrodifferential equations, 685, 695  
 International System of Units, 4, 5, 21  
 Inverse Fourier transform, 762, 789  
 Inverse Laplace transform, 647, 648, 695  
   steps for finding, 659  
 Inverting amplifier; *see* Amplifier  
 Irwin, J. D., 929

## J

Jackson, H. W., 929  
 Johnson, D. E., 929

## K

Karni, S., 929  
 Katz, L., 929  
 Kemmerly, J. E., 929  
 Kinariwala, B. K., 930  
 Kirchhoff, G. Robert, 27, 35  
 Kirchhoff's laws, 35  
 Kirchhoff's current law (KCL), 36, 61, 372, 394  
   definition of, 36  
   in frequency domain, 372  
 Kirchhoff's voltage law (KVL), 37, 61, 373, 397  
   definition of, 37  
 Kraus, A. D., 929

## L

Ladder method, 673  
 Ladder network, 831, 834  
 Lagging, 356, 368, 370  
   power factor, 448  
 Laplace, P. Simon, 645  
 Laplace transform, 645, 646, 694  
   applications of, 687  
   definition of, 646  
   properties of, 649–656  
   steps for applying, 667  
 Lawson, W., 929  
 Leach, D. P., 929  
 Leading, 356, 368, 370  
   power factor, 448  
 L'Hopital's rule, 863  
 Lighting system, 55  
 Lin, P. M., 929  
 Lin, P. Y., 929  
 Line current, 484, 487, 489, 491, 492, 500, 517

Line spectra, 736  
 Line voltage, 483, 484, 486, 489, 490, 492  
 Linear circuit, 120, 153  
   definition of, 121  
 Linear capacitor, 204  
 Linearity, 120, 333, 649, 766  
 Load, 57  
   balanced type, 481  
   three-phase type, 481  
   unbalanced type, 481  
 Loading effect, 148  
 Logarithm, 588  
 Loop, 34, 87  
   definition of, 34  
 Loop analysis; *see* Mesh analysis  
 Lowpass filter, 609, 614, 629, 630  
   definition of, 610

## M

Madhu, S., 929  
 Magnetic coupling, 528, 529  
   loosely type, 537  
   perfect type, 537, 545  
   tightly type, 537  
 Magnitude, 585  
 Maloney, T. J., 929  
 Maximum power transfer, 153, 556  
   for AC circuits, 440, 441  
   for DC circuits, 142–144  
 Mayergoyz, I. D., 929  
 Mesh, 87  
   definition of, 88  
 Mesh analysis, 87, 92, 397  
   by inspection, 95–96  
   versus nodal analysis, 99  
   steps for, 89  
 Method of algebra, 662  
 Morse, Samuel, 150, 645  
 Mottershead, A., 930  
 Multimeter, 57  
 Mutual inductance, 528–530, 539, 569  
   definition of, 530  
 Mutual voltage, 529, 530, 569

## N

Napier, John, 303  
 Nasar, S. A., 930  
 National Electrical Code (NEC), 515  
 Natural response, 239, 259, 282, 301, 303, 314, 320, 340  
   definition of, 239  
 Negative sequence; *see* ACB sequence  
 Netlist, 873  
 Network, 33  
   balanced type, 52, 375

Network stability, 687, 695  
 definition of, 688  
 Network synthesis, 691, 695, 630  
 definition of, 691  
 Network topology, 33, 34  
 Neudorfer, P. O., 930  
 Nilsson, J. W., 930  
 Nodal analysis, 76, 82, 394  
 by inspecton, 95  
 versus mesh analysis, 99  
 steps for, 76  
 Node, 33  
 Noninverting amplifier; *see* Amplifier  
 Norton's theorem, 137, 138, 153, 406  
 definition of, 137  
 derivation of, 140  
 with *PSpice*, 144  
 Notch filter; *see* Bandstop filter  
 Nyquist frequency/rate, 789, 790

## O

Odd function, 720  
 Ohm, Georg, 27, 29  
 Ohm's law, 28, 779  
 definition of, 29  
 Ohmmeter, 59  
 O'Malley, J. R., 930  
 Op amp, 166  
 applications of, 185  
 definition of, 166  
 first-order circuit, 268  
 ideal type, 170, 189  
 properties of, 170, 411  
 with *PSpice*, 183  
 second-order circuit, 327  
 Open circuit, 30, 60  
 definition of, 30  
 Operational amplifier; *see* Op amp  
 Oscillation, 305, 306  
 Oscillator, 418, 420, 627, 689  
 definition of, 418  
 types of, 431  
 Oscilloscope, 223, 746, 867  
 Overdamped response; *see* Response

## P

Papoulis, A., 930  
 Parallel combination, 61  
 of capacitors, 229, 208  
 definition of, 34  
 of impedances, 374  
 of inductors, 233, 215  
 of resistors, 43  
 of two-ports, 818

Parameters, 796  
 admittance or  $y$  type, 801  
 computation with *PSpice*, 823  
 hybrid or  $h$  type, 805, 827  
 immittance type, 801  
 impedance or  $z$  type, 796, 797  
 inverse hybrid or  $g$  type, 805  
 inverse transmission or **abcd** type, 811  
 transmission or **ABCD** type, 810  
 Parrett, R., 930  
 Parseval, Marc-Antonie, 732  
 Parseval theorem, 732, 735, 751, 782, 789  
 Partial fraction expansion, 659  
 Passive filters, 608  
 limitations of, 613  
 Passive sign convention, 10, 22, 874  
 for capacitor, 203  
 definition of, 10  
 for inductor, 212  
 for mutual voltage, 530  
 for resistor, 29  
 Paul, C. R., 930  
 Period, 355, 356  
 Periodic function, 355, 654, 708, 746, 749  
 definition, 355  
 Phase, 356, 384, 585  
 Phase current, 484, 485, 487, 491, 492, 494, 517  
 Phase diagram, 481  
 Phase voltage, 480, 484, 486, 489, 490, 492, 494, 517  
 balanced type, 480  
 Phase sequence, 481, 516  
 definition of, 481  
 Phase-shifters, 379  
 Phase spectrum, 711, 735, 762  
 Phasor, 359, 361–363, 384  
 definition of, 359  
 Phasor diagram, 362, 368, 369, 487  
 Phasor domain, 363  
 Phasor representation, 361  
 of circuit elements, 367–368  
 Poles, 585, 591, 631, 659, 688  
 definition of, 585  
 Polyphase, 478  
 Port, 796  
 Positive sequence; *see* ABC sequence  
 Pot; *see* Potentiometer  
 Potential difference; *see* Voltage  
 Potentiometer, 56  
 Poularikas, A. D., 930  
 Power, 10, 22, 31, 121, 123, 333, 731, 732  
 apparent power, 447, 451, 465  
 average, 435, 445, 464  
 complex, 449, 465  
 conservation of, 11, 453  
 definition of, 10  
 instantaneous, 10, 434, 464  
 reactive, 450, 451, 465  
 Power distribution, 567  
 Power factor, 447, 451, 462, 464, 509, 510  
 definition of, 448  
 Power factor angle, 447, 450, 451, 510

Power factor correction, 457, 458, 465  
 definition of, 457  
 Power grid, 568  
 Power measurement, 459  
 for three-phase systems, 508  
 Power spectrum, 735  
 Power systems, 433, 567  
 Power triangle, 451  
 Probe, 866  
 Problem solving, 18–21  
 PSpice, 100, 107, 144, 153, 865  
 for AC analysis, 413  
 for coupled circuits, 559  
 for DC analysis, 872  
 for Fourier analysis, 740  
 for frequency response, 622  
 for op amp, 183  
 for three-phase systems, 504  
 for two-port parameters, 823  
 transient analysis, 273, 283, 330, 340

## Q

Quadratic formula, 859  
 Quality factor, 603, 616, 620, 632  
 definition of, 603

## R

Radio receiver, 626, 632  
 Reactance, 370  
 Reactive power, 450, 451, 465, 495, 510, 556  
 Real power, 451, 464, 517, 556; *see also* Average power  
 Rectifier, 564  
 Reference node, 76  
 Reflected impedance, 541, 548  
 Relay circuit, 280  
 Residential wiring, 514  
 Residue method, 660  
 Resistance, 28, 60  
 definition of, 29, 390  
 Resistance matrix, 96  
 Resistance measurement, 150, 153  
 Resistivity, 28  
 Resistor, 28,  
 applications of, 54  
 types of, 30  
 Resonance  
 definition of, 601  
 parallel type, 605  
 series type, 600  
 Resonant circuit, 601, 603, 604  
 applications of, 626  
 Resonant frequency, 601, 620, 632  
 Response, 120, 677  
 critically damped, 303, 315, 340

overdamped, 303, 315, 340  
 underdamped, 304, 315, 340  
 Reversal, 770  
 RC circuit, 238  
 applications of, 276, 278  
 Ringing, 305, 306  
 Ridsdale, R. E., 930  
 Riedel, S. A., 930  
 RL circuit, 243  
 applications of, 280, 281  
 RLC circuit, 296, 340  
 applications of, 336, 338  
 parallel type, 308, 319  
 properties of, 305  
 series type, 301, 314  
 RMS; *see* Root-mean-square  
 Root-mean-square (*rms*) value, 730, 731, 750; *see also*  
 Effective value  
 Rosa, A. J., 930

## S

Sampling, 338, 788, 790  
 Sampling function, 736  
 Sampling rate, 788  
 Sampling theorem, 746, 788  
 Sander, K. F., 930  
 Sawtooth function, 254  
 Scaling, 619, 632, 649, 767  
 frequency type, 620, 621  
 magnitude type, 619, 621  
 Schematics, 866, 867  
 Scott, D., 930  
 Second-order circuits, 296, 302, 322, 327, 340  
 definition of, 296  
 Selectivity, 603  
 Self-inductance, 529  
 Series combination, 61  
 of capacitors, 229, 209  
 definition of, 34  
 impedances, 373  
 of inductors, 233, 216  
 of resistors, 42  
 of two-ports, 817  
 Short circuit, 29, 60  
 definition of, 30  
 SI unit; *see* International System of Units  
 Signal, 9  
 Signum function, 776  
 Simulation, 865, 866, 882, 887  
 Sinc function, 736  
 Singularity functions, 249  
 definition of, 249  
 Sinor, 361  
 Sinusoid, 354  
 definition of, 354  
 Smith, K. C., 930  
 Smoothing circuit, 338, 340  
 Software engineering, 393

- Source
  - dependent type, 13, 22
  - ideal type, 13, 14, 22
  - independent type, 13, 22
- Source-free circuits, 238
  - RC* type, 238
  - RL* type, 243
  - RLC* type, 301, 308
- Source modeling, 147, 153, 154
- Source resistance, 148
- Source transformation, 127, 128, 129, 138, 153, 404
- Spectrum analyzer, 746, 747, 751
- Stanley, W. D., 930
- Steady-state response, 259; *see also* Forced response
- Steinmetz, C. Proteus, 353, 359
- Step response, 257, 283, 322
  - definition of, 258
  - of *RC* circuit, 257
  - of *RL* circuit, 263
  - of *RLC* circuit, 314, 319
- Storage elements, 202
- Strum, R. D., 930
- Stuller, J. A., 929
- Subtractor, 177, 178
- Summing amplifier; *see* Amplifier
- Summer, 176; *see also* Amplifier, summing type
- Supermesh, 92, 107, 399
  - definition of, 92
  - properties of, 93
- Supernode, 83, 107, 396
  - definition of, 83
  - properties of, 84
- Superposition, 122, 140, 153, 400, 420
  - definition of, 123
- Susceptance, 371
- Svoboda, J. A., 929
- Sweeps, 622
  - types of, 622
- Switching functions; *see* Singularity functions
- Symmetry, 717
  - even type, 717
  - half-wave type, 720
  - odd type, 719
- Synthesis; *see* Network synthesis
- Time differentiation, 651, 769
- Time integration, 652, 770
- Time periodicity, 654
- Time scaling, 767
- Time shifting, 650, 768
- Tocci, R. J., 930
- Total response, 400; *see also* Complete response
- Touch-tone telephone, 628, 633
- Transfer admittance, 585, 672
- Transfer function, 584, 589, 631, 672–673, 691, 695, 779, 789
  - definition of, 584, 672, 673
- Transfer impedance, 585, 672
- Transformer, 338, 528, 569
  - air-core type, 540, 569
  - applications of, 528, 546
  - definition of, 539
  - ideal type, 545, 546, 570, 798
  - isolation type, 547, 564
  - linear type, 539, 540, 569
  - matching type, 566
  - step-down type, 547
  - step-up type, 547
  - three-phase type, 556, 570
  - types of, 564
- Transient response, 259, 282
  - with *PSpice*, 273
- Transistor, 102–104, 107, 826, 834
- Transmission lines, 479
- Trigonometric identities, 859
- Tuinenga, P. W., 930
- Turns ratio, 546
- TV picture tube, 15, 22
- Two-phase system, 478
- Two-port network, 796, 833
  - applications of, 826, 830
  - definition of, 796
  - interconnection of, 817
  - reciprocal type, 798, 834
  - symmetrical type, 798
- Two-port network parameters; *see* Parameters
- Two-wattmeter method, 509, 517
- Two-wire system, 478, 495

## T

- Tesla, Nikola, 447
- Thevenin theorem, 131–133, 137, 153, 406
  - definition of, 131
  - derivation of, 140
  - with *PSpice*, 144
- Thomas, R. E., 930
- Three-phase system, 478, 479, 496
- Three-wattmeter method, 508
- Three-wire system, 478, 496
- Time constant, 239–241, 244, 277, 278, 281, 282
  - definition of, 240

## U

- Unbalanced load, 481
- Unbalanced system, 500, 517
  - definition of, 500
- Underdamped response; *see* Response
- Unit impulse, 251, 283
  - definition of, 251
  - sifting property of, 252
- Unit ramp, 252, 283
  - definition of, 252
- Unit step, 250, 282
  - definition of, 250

## V

Van Valkenburg, M. E., 930  
Varmeter, 459  
Volta, Alessandro Antonio, 3, 9  
Voltage, 9, 22  
Voltage divider, 42  
Voltage division, 229, 233, 42, 56, 61, 373  
Voltage follower, 174, 189, 416  
Voltage gain, 585, 672  
Voltmeter, 57  
    sensitivity of, 60

## W

Ward, J. R., 930  
Wattmeter, 435, 459, 465, 508  
    definition of, 460

Wheatstone, Charles, 150  
Wheatstone bridge, 150, 153  
White, P. A., 929  
Whitehouse, J. E., 930  
Wye-connected load, 492, 482, 490  
Wye-connected source, 482, 486  
Wye-delta transformation, 50, 51, 61, 375

## Y

Yorke, R., 930

## Z

Zeros, 585, 591, 631, 659, 688  
    definition of, 585